

Measuring Transistor Characteristic Curves

David W. Body


March 14, 2024

This note documents how to measure transistor characteristic curves using an oscilloscope as described in (Buyl 2010). The circuit is also based on Lab 33 in (Buchla 2010).

The collector-emitter characteristic curves for a bipolar junction transistor show how collector current, I_C , varies with the collector-emitter voltage, V_{CE} , for various specified values of base current, I_B .

In this case, we use a 2N3904 NPN bipolar junction transistor.

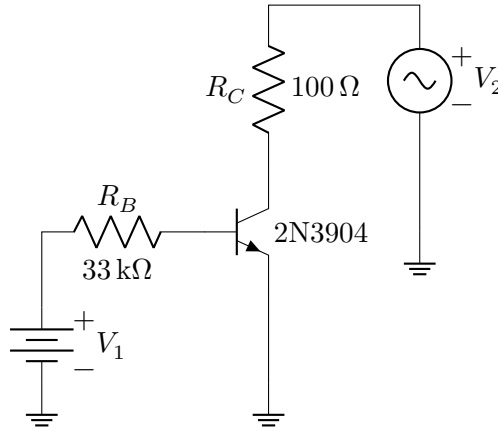We can measure transistor characteristics using the following circuit



where V_1 is a DC voltage source that can be set to various voltages that will determine the base current, I_B . In this circuit,

$$I_B \approx \frac{V_1}{R_B} = \frac{V_1}{33\text{ k}\Omega}$$

For a given voltage, V_1 , we can trace out a characteristic curve by setting V_2 to a sawtooth waveform with a frequency of 100 Hz and voltage of 0V to 10V.

The characteristic curve is I_C as a function of V_{CE} . In this circuit

$$I_C = \frac{V_2 - V_{CE}}{R_C}$$

We connect the oscilloscope channel 1 at the top of R_C , and channel 2 at the collector. This lets us measure

$$V_2 = V_{CH1}$$

and

$$I_C = \frac{V_{CH1} - V_{CH2}}{R_C} = \frac{V_{CH1} - V_{CH2}}{100\Omega}$$

where V_{CH1} and V_{CH2} are the measured channel 1 and channel 2 voltages, respectively.

Each cycle of the sawtooth waveform V_2 traces out a characteristic curve.

We set the DC voltage source V_1 to the following voltages:

0.5V, 1.0V, 1.5V, 2.0V, 2.5V, 3.0V, 3.5V, 4.0V, 4.5V, 5.0V

For each of these, we capture the output of the oscilloscope as a CSV file.

Here is a representative set of waveforms from the oscilloscope for $V_1 = 2.5V$.



We then use R to read the oscilloscope data, from which we can compute and plot the characteristic curves.

This is the code to read and combine the CSV files.

```
library(tidyverse)
```

```
V1_05 <- read_csv("2N3904/RigolDS0.csv", col_types = "dd??")
V1_05$V1 <- 0.5

V1_10 <- read_csv("2N3904/RigolDS1.csv", col_types = "dd??")
V1_10$V1 <- 1.0

V1_15 <- read_csv("2N3904/RigolDS2.csv", col_types = "dd??")
V1_15$V1 <- 1.5

V1_20 <- read_csv("2N3904/RigolDS3.csv", col_types = "dd??")
V1_20$V1 <- 2.0

V1_25 <- read_csv("2N3904/RigolDS4.csv", col_types = "dd??")
V1_25$V1 <- 2.5

V1_30 <- read_csv("2N3904/RigolDS5.csv", col_types = "dd??")
V1_30$V1 <- 3.0

V1_35 <- read_csv("2N3904/RigolDS6.csv", col_types = "dd??")
V1_35$V1 <- 3.5

V1_40 <- read_csv("2N3904/RigolDS7.csv", col_types = "dd??")
V1_40$V1 <- 4.0


V1_45 <- read_csv("2N3904/RigolDS8.csv", col_types = "dd??")
V1_45$V1 <- 4.5

V1_50 <- read_csv("2N3904/RigolDS9.csv", col_types = "dd??")
V1_50$V1 <- 5.0

t_df <- rbind(V1_05, V1_10, V1_15, V1_20, V1_25,
              V1_30, V1_35, V1_40, V1_45, V1_50)
```

Finally, we compute I_B , I_C , and V_{CE} , and plot the curves.

```
t_df |>
  mutate(IB = as.factor(round((V1 / 33000)*1e6)),
         IC = ((CH1V - CH2V)/100)*1000, VCE = CH2V) |>
  ggplot(aes(VCE, IC, color = fct_reorder2(IB, VCE, IC))) +
  geom_line() +
  labs(title = "Transistor characteristic curves",
       subtitle = "2N3904",
       x = expression(paste(V[CE], " (V)")),
       y = expression(paste(I[C], " (mA)")),
       color = expression(paste(I[B], " (A)"))) +
  theme_minimal()
```

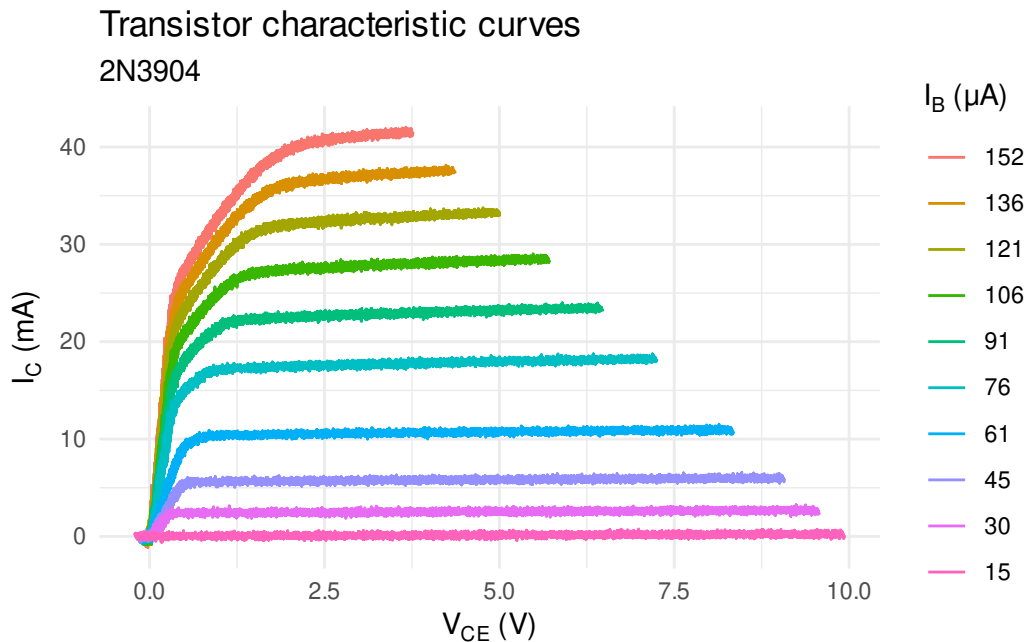

References

- Buchla, David M. 2010. *Experiments in Electronics Fundamentals and Electric Circuits Fundamentals*.
- Buyl, Pierre de. 2010. "A Digital Oscilloscope Setup for the Measurement of a Transistor's Characteristics." *arXiv*. <https://doi.org/10.48550/ARXIV.1006.0954>.